

디지털 공학 (MEC520)

Final Examination

Spring, 2009

1. Design a 4-input priority encoder with input D0 (the Lowest Significant Bit) having the highest priority and input D3 (the Highest Significant Bit) having the lowest priority. Assume that x, y are outputs, and y is the Lowest Significant Bit. Don't care the outputs when all 4-inputs are zero. (20pt)

2. Design the negative edge triggered synchronous 3-bit binary counter using D flip-flops and one input x, count up when $x=1$, and count down when $x=0$. (20pt)

3. Explain functions of the following logic when the inputs to the MUX change. (20pt)

 


Fig. 6-7 4-Bit Universal Shift Register

4. Fill out three blanks with proper VHDL codes. (20pt)

5. Obtain the input Boolean functions for a synchronous counter with the following repeated binary sequence: 0, 1, 2, 4, 6. Use JK flip-flops. And obtain the next number when it start at 3, 5 or 7 (20pt)

EX_5_3_V.vhd

```
LIBRARY IEEE;
USE IEEE.STD_LOGIC_1164.ALL;

ENTITY EX_5_3_V IS
    PORT(
        RST, SI, CLK : IN STD_LOGIC;
        REG          : OUT STD_LOGIC_VECTOR(7 DOWNTO 0));
END EX_5_3_V;

ARCHITECTURE BF OF EX_5_3_V IS
    SIGNAL SR : ( _____ )
( _____ ) DIFF_RST
    PORT(
        D, RST, CLK : IN STD_LOGIC;
        Q           : OUT STD_LOGIC);
END COMPONENT;

BEGIN
    DF7 : DIFF_RST PORT MAP(SI, RST, CLK, SR(7));
    DF6 : DIFF_RST PORT MAP(SR(7), RST, CLK, SR(6));
    DF5 : DIFF_RST PORT MAP(SR(6), RST, CLK, SR(5));
    DF4 : DIFF_RST PORT MAP(SR(5), RST, CLK, SR(4));
    DF3 : DIFF_RST PORT MAP(SR(4), RST, CLK, SR(3));
    DF2 : DIFF_RST PORT MAP(SR(3), RST, CLK, SR(2));
    DF1 : DIFF_RST PORT MAP(SR(2), RST, CLK, SR(1));
    DF0 : DIFF_RST PORT MAP(SR(1), RST, CLK, SR(0));
    REG <= SR;
END BF;
```

DIFF_RST.vhd

```
LIBRARY IEEE;
USE IEEE.STD_LOGIC_1164.ALL;

ENTITY DIFF_RST IS
    PORT(
        D, RST, CLK : IN STD_LOGIC;
        Q           : OUT STD_LOGIC);
END DIFF_RST;

ARCHITECTURE BF OF DIFF_RST IS
BEGIN
PROCESS(RST, CLK)
BEGIN
    IF RST = '0' THEN Q <= '0';
    ELSIF ( _____ ) THEN Q <= D; --when rising edge
    END IF;
END PROCESS;
END BF;
```

디지털 공학 (MEC520)
Final Examination

Spring, 2009

학번 _____

이름 _____